

Verilog HDL: User Defined Primitives

Pravin Zode

Outline

- UDP Introduction
- Types of UDP
- Rules for defining UDP
- Combinational UDP
- Sequential UDP

Introduction

- Verilog includes built-in primitives like and, or, not, nand, nor, etc.
- Designers can also create custom logic blocks called User-Defined Primitives (UDPs)
- Instantiated just like gate-level primitives in the design
- Useful for abstracting small logic blocks without full modules

Types of UDP

- **Combinational UDPs:**

- Output depends only on current inputs.
- Example: 4-to-1 Multiplexer

- **Sequential UDPs:**

- Output depends on current inputs + current output (state).
- Output acts as the internal state.
- Examples: Latches, Flip-Flops.

UDP Definition

```
//UDP name and terminal list  
primitive <udp_name> (  
  <output_terminal_name> (only one allowed)  
  <input_terminal_names> );
```

```
//Terminal declarations  
output <output_terminal_name>;  
input <input_terminal_names>;  
reg <output_terminal_name>; (optional; only for sequential  
                                UDP)
```

```
// UDP initialization (optional; only for sequential UDPs)  
initial <output_terminal_name> = <value>;
```

```
//UDP state table  
table  
  <table entries>  
endtable
```

```
//End of UDP definition  
endprimitive
```

Rules for defining UDP

- Scalar Inputs Only
 - All input terminals must be 1-bit (scalar)
 - Multiple inputs are allowed
- Single Scalar Output
 - Only one 1-bit output terminal is permitted
 - Output must appear first in the terminal list
- Output Declaration
 - Declared using the keyword **output**
 - In sequential UDPs, it must also be declared as **reg**.
- Input Declaration
 - Inputs are declared using the **input** keyword

Rules for defining UDP

- initial statement can be used to initialize state (output)
- This is optional and assigns a 1-bit value to the output
- Valid State Table Values : Allowed entries: 0, 1, X
- z values are not supported and treated as X
- UDPs must be defined at the same level as modules
- Cannot be defined inside modules, but can be instantiated inside them.
- Do not support inout ports
- These rules apply to combinational and sequential UDPs a

Example

```
1  ✓ primitive udp_example (out, in1, in2);  
2      output out;  
3      input in1, in2;  
4  ✓  table  
5      0 0 : 0;  
6      0 1 : 1;  
7      1 0 : 1;  
8      1 1 : 0;  
9      endtable  
10 endprimitive
```


Example : Adder

```
1  // -----
2  // Full Adder Sum Generation using UDP
3  // sum = a ^ b ^ c
4  //-----
5  primitive udp_sum (sum, a, b, c);
6      input a, b, c;
7      output sum;
8
9      table
10         // a b c : sum
11         0 0 0 : 0;
12         0 0 1 : 1;
13         0 1 0 : 1;
14         0 1 1 : 0;
15         1 0 0 : 1;
16         1 0 1 : 0;
17         1 1 0 : 0;
18         1 1 1 : 1;
19     endtable
20
21 endprimitive
```

```
1  // -----
2  // Full Adder Carry Generation UDP
3  // cout = (a & b) | (b & c) | (a & c)
4  // -----
5  primitive udp_cy (cout, a, b, c);
6      input a, b, c;
7      output cout;
8
9      table
10         // a b c : cout
11         0 0 0 : 0;
12         0 0 1 : 0;
13         0 1 0 : 0;
14         0 1 1 : 1;
15         1 0 0 : 0;
16         1 0 1 : 1;
17         1 1 0 : 1;
18         1 1 1 : 1;
19     endtable
20
21 endprimitive
```

Example : Adder (Instantiation)

```
1  // -----  
2  // Full Adder Implementation by Instantiating UDPs  
3  // SUM = a ^ b ^ c  
4  // COUT = (a & b) | (b & c) | (a & c)  
5  // -----  
6  
7  ✓ module full_adder (sum, cout, a, b, c);  
8      input a, b, c;  
9      output sum, cout;  
10  
11     // Instantiate UDP for sum  
12     udp_sum  SUM  (sum, a, b, c);  
13  
14     // Instantiate UDP for carry  
15     udp_cy   CARRY (cout, a, b, c);  
16 endmodule
```

Rules for State Table Entries

- Input Order is Crucial : Inputs in the state table must appear in the same order as listed in the terminal definition
- Inputs and output in the state table are separated by a colon (:).
- Each state table entry must end with a semicolon (;)
All valid input combinations that produce a known output must be explicitly written.
- Define all possible combinations, especially those involving X values, to avoid ambiguous outputs.

UDP with Don't care

```
1  primitive udp_or (out, a, b);
2      output out;
3      input a, b;
4
5      table
6      // a  b : out
7          0  0 : 0;
8          0  1 : 1;
9          1  0 : 1;
10         1  1 : 1;
11
12         0  x : x;  // optional: or define 0 x : x;
13         x  0 : x;
14         1  x : 1;  // logic holds if one input is 1
15         x  1 : 1;
16         x  x : x;
17     endtable
18 endprimitive
```

UDP with Don't care shortcut

```
1  primitive udp_or (out, a, b);
2      output out;
3      input a, b;
4
5      table
6      // a  b : out
7          0  0 : 0;
8          ?  1 : 1;
9          1  ? : 1;
10         x  0 : x;
11         0  x : x;
12         x  x : x;
13     endtable
14 endprimitive
```

- ? means 0, 1, or x → "don't care" for matching purposes.
- So:
- ? 1 : 1; covers {0 1}, {1 1}, {x 1}
- 1 ? : 1; covers {1 0}, {1 1}, {1 x}

Example: Combinational UDPs

```
1  primitive comb_udp (out, a, b);
2      output out;
3      input a, b;
4      table
5          // a  b  : out
6          0  0  : 0;
7          0  1  : 1;
8          1  0  : 1;
9          1  1  : 0;
10     endtable
11 endprimitive
12
13 module tb_comb_udp;
14     reg a, b;
15     wire out;
16     comb_udp uut(out, a, b);
17     initial begin
18         $monitor("At time %0t: a=%b, b=%b, out=%b", $time, a, b, out);
19         a = 0; b = 0; #10;
20         a = 0; b = 1; #10;
21         a = 1; b = 0; #10;
22         a = 1; b = 1; #10;
23     end
24 endmodule
```

Expected Output:

```
At time 0: a=0, b=0, out=0
At time 10: a=0, b=1, out=1
At time 20: a=1, b=0, out=1
At time 30: a=1, b=1, out=0
```

Example: UDP Instance

```
1 module udp_instance;
2   reg a, b;
3   wire y;
4   comb_udp my_udp (y, a, b);
5 endmodule
```


```
7 module tb_udp_instance;
8   reg a, b;
9   wire y;
10  comb_udp uut (y, a, b);
11  initial begin
12    $monitor("At time %0t: a=%b, b=%b, y=%b", $time, a, b, y);
13    a = 0; b = 0; #10;
14    a = 0; b = 1; #10;
15    a = 1; b = 0; #10;
16    a = 1; b = 1; #10;
17    $finish;
18  end
19 endmodule
```

```
- primitive comb_udp (out, a, b);
-   output out;
-   input a, b;
-   table
-       // a b : out
-       0 0 : 0;
-       0 1 : 1;
-       1 0 : 1;
-       1 1 : 0;
-   endtable
- endprimitive
```

Expected Output:

```
At time 0: a=0, b=0, y=0
At time 10: a=0, b=1, y=1
At time 20: a=1, b=0, y=1
At time 30: a=1, b=1, y=0
```

Example: Combinational UDPs

 

S1	S0	Out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

```
// 4-to-1 multiplexer. Define it as a primitive
primitive mux4_to_1 (out, i0, i1, i2, i3, s1, s0);
```

```
// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;
```

```
table
    // i0 i1 i2 i3, s1 s0 : out
        1 ? ? ? 0 0 : 1 ;
        0 ? ? ? 0 0 : 0 ;
        ? 1 ? ? 0 1 : 1 ;
        ? 0 ? ? 0 1 : 0 ;
        ? ? 1 ? 1 0 : 1 ;
        ? ? 0 ? 1 0 : 0 ;
        ? ? ? 1 1 1 : 1 ;
        ? ? ? 0 1 1 : 0 ;
        ? ? ? ? x ? : x ;
        ? ? ? ? ? x : x ;
endtable

endprimitive
```


Sequential UDPs

- Sequential UDP must be declared as reg, since it stores state Uses internal state (reg) to store values
- A sequential UDP may use an initial block to initialize the output value before simulation starts
- State Table Format:
- Three fields separated by colons (:)
 - Inputs
 - Current state (value of the output reg)
 - Next state
- Example format:
1 0 : 0 : 1; (Input = 1 0, Current State = 0, Next State = 1)

Sequential UDPs

Input Specification Types:

- Level-sensitive: Responds to input values (like 0 or 1)
- Edge-sensitive: Responds to input transitions ((01), (10), etc.)

Next State Logic:

- Determined based on inputs + current state
- The next state becomes the output for the next evaluation

Sequential UDPs

Complete Specification Required:

- Must define all valid combinations of input + current state to avoid unknown (X) results.
- Incomplete tables result in unpredictable outputs during simulation

Level-sensitive vs Edge-sensitive:

- Level-sensitive UDP: Behaves like latches
- Edge-sensitive UDP: Behaves like flip-flops (e.g., D flip-flop triggered on clock edge).

UDP Table Symbols

Shorthand Symbols	Meaning	Explanation
?	0, 1, x	Cannot be specified in an output field
b	0, 1	Cannot be specified in an output field
-	No change in state value	Can be specified only in output field of a sequential UDP
r	(01)	Rising edge of signal
f	(10)	Falling edge of signal
p	(01), (0x) or (x1)	Potential rising edge of signal
n	(10), (1x) or (x0)	Potential falling edge of signal
*	(??)	Any value change in signal

UDP Table Symbols

```
table
  // d clock clear : q : q+ ;

  ?   ?   1   : ? : 0 ; //output = 0 if clear = 1
  ?   ?   f   : ? : - ; //ignore negative transition of clear

  1   f   0   : ? : 1 ; //latch data on negative transition of
  0   f   0   : ? : 0 ; //clock

  ?   (1x) 0   : ? : - ; //hold q if clock transitions to unknown
                          //state

  ?   p   0   : ? : - ; //ignore positive transitions of clock

  *   ?0   : ? : - ; //ignore any change in d when
                      //clock is steady
endtable
```

Example : Level-Sensitive Sequential UDPs

```
1  primitive level_seq_udp (out, clk, d);
2      output out;
3      reg out;
4      input clk, d;
5      table
6          // clk  d  : state : new_state
7          | 0   ?  :   ?   :   -   ; // No change when clk = 0
8          | 1   0  :   ?   :   0   ;
9          | 1   1  :   ?   :   1   ;
10     endtable
11 endprimitive

12
13 module tb_level_seq_udp;
14     reg clk, d;
15     wire out;
16     level_seq_udp uut(out, clk, d);
17     initial begin
18         clk = 0; d = 0;
19         #5 clk = 1; d = 1;
20         #5 clk = 0;
21         #5 clk = 1; d = 0;
22         #5 clk = 0;
23     end
24     initial $monitor("At time %0t: clk=%b, d=%b, out=%b", $time, clk, d, out);
25 endmodule
```

Expected Output:

At time 5: clk=1, d=1, out=1
At time 15: clk=1, d=0, out=0

Example : Level-Sensitive Sequential UDPs

```
1  // Define level-sensitive latch using a sequential UDP
2  primitive latch(q, d, clock, clear);
3  // Output declaration
4  output q;
5  reg q; // 'q' must be reg for sequential UDP
6  // Input declaration
7  input d, clock, clear;
8  // Initialize output
9  initial
10 |   q = 0; // Set initial value of q
11 // State table definition
12 // Format: d clock clear : current_state : next_state ;
13 table
14 |   // Clear active (asynchronous clear)
15 |   ? ? 1 : ? : 0 ; // Clear overrides everything
16 |   // Latch behavior when clock is high and clear is low
17 |   1 1 0 : ? : 1 ; // Latch data = 1
18 |   0 1 0 : ? : 0 ; // Latch data = 0
19 |   // Retain value when clock is low and clear is inactive
20 |   ? 0 0 : ? : - ; // Hold previous state
21 endtable
22 endprimitive
```

Example : Edge-Sensitive Sequential UDPs

```
1  primitive edge_seq_udp (out, clk, d);
2      output out;
3      reg out;
4      input clk, d;
5      table
6          // clk d : state : new_state
7          | (01) 0 : ? : 0;
8          | (01) 1 : ? : 1;
9      endtable
10 endprimitive
```

```
11
12 module tb_edge_seq_udp;
13     reg clk, d;
14     wire out;
15     edge_seq_udp uut(out, clk, d);
16     initial begin
17         clk = 0; d = 0;
18         #5 clk = 1; d = 1;
19         #5 clk = 0;
20         #5 clk = 1; d = 0;
21         #5 clk = 0;
22     end
23     initial $monitor("At time %0t: clk=%b, d=%b, out=%b", $time, clk, d, out);
24 endmodule
```

Expected Output:

```
At time 5: clk=1, d=1, out=1
At time 15: clk=1, d=0, out=0
```


Example : Edge-Sensitive Sequential UDPs

```
1  // Define an edge-sensitive sequential UDP (D Flip-Flop with asynchronous clear)
2  primitive edge_dff(q, d, clock, clear);
3  // Declarations
4  output q;
5  reg q; // Must be reg to store state
6  input d, clock, clear;
7  // Initialization
8  ∨ initial
9  |     q = 0;
10 // State table
11 // Format: d clock clear : q : q+ ;
12 ∨ table
13 |     ? ?      1 : ? : 0 ;    // Asynchronous clear
14 |     ? ? (10) : ? : - ;    // Ignore negative edge of clear
15 |     1 (10)   0 : ? : 1 ;    // Capture data=1 on rising edge of clock
16 |     0 (10)   0 : ? : 0 ;    // Capture data=0 on rising edge of clock
17 |     ? (1x)   0 : ? : - ;    // Hold output if clock becomes unknown after 1
18 |     ? (0?)   0 : ? : - ;    // Ignore positive transitions
19 |     ? (x1)   0 : ? : - ;    // Ignore positive transitions
20 |     (??)     ? : ? : - ;    // Ignore changes in 'd' when clock is steady
21
22 endtable
23 endprimitive
```

Example : Sequential UDPs (T-FF)

```
1  // Edge-triggered T-flipflop using UDP
2  primitive T_FF(q, clk, clear);
3
4  // Output and input declarations
5  output q;
6  reg q;
7  input clk, clear;
8
9  // No initialization needed; TFF is initialized using clear signal
10
11  table
12  // clk  clear : q : q+ ;
13  |      ?      1      : ? : 0 ;      // Asynchronous clear
14  | (10)    0      : 1 : 0 ;      // Toggle q on rising edge if q is 1 -> becomes 0
15  | (10)    0      : 0 : 1 ;      // Toggle q on rising edge if q is 0 -> becomes 1
16  | (0?)    0      : ? : - ;      // Ignore positive transitions
17  endtable
18
19  endprimitive
```

Example : Sequential UDPs (Counter)

```
1  module counter(Q, clock, clear);
2      output [3:0] Q;
3      input clock, clear;
4
5      // Instantiate 4 T flip-flops
6      T_FF tff0(Q[0], clock, clear);
7      T_FF tff1(Q[1], Q[0], clear);
8      T_FF tff2(Q[2], Q[1], clear);
9      T_FF tff3(Q[3], Q[2], clear);
10 endmodule
```

```
1  `timescale 1ns / 1ps
2  module tb_counter;
3      reg clk, clr;
4      wire [3:0] Q;
5
6      // Instantiate the counter
7      counter uut(Q, clk, clr);
8      // Clock generation
9      initial begin
10         clk = 0;
11         forever #5 clk = ~clk;
12         // 10ns clock period
13     end
14     // Stimulus
15     initial begin
16         $dumpfile("counter.vcd");
17         $dumpvars(0, tb_counter);
18
19         clr = 1; #10;
20         clr = 0; #200;
21
22         $finish;
23     end
24 endmodule
```

Summary

- User-Defined Primitives (UDP) allow creation of custom Verilog primitives using lookup tables
- UDPs are useful for defining simple, functional blocks in a concise format
- A UDP can have only one output terminal and must be defined at the same level as modules
- UDPs are instantiated like gate-level primitives (e.g., and, or)
- The state table is the core part of a UDP definition.



Thank you !

Happy Learning