

# Verilog HDL: FSMD & ASMD

**Pravin Zode**

# Outline

- Introduction
- Why Finite State Machine with Datapath (FSMD)
- Block diagram
- Components and functions of FSMD
- Comparison with FSM and FSMD
- FSMD Example
- ASMD

# What is FSMD ?


- A Finite State Machine with Datapath (FSMD) is an extension of a traditional FSM that includes a datapath along with the control logic
- Unlike traditional FSMs, FSMD can process arithmetic and logical operations alongside state transitions
- The control unit dictates operations on the datapath based on the current state and inputs
- Suitable for complex digital system designs that require computation and decision-making

# Why FSM ?

- Structured design: Separation of control and data
- Handles sequential operations effectively
- Suitable for hardware implementation (HDLs)
- Wide range of applications.
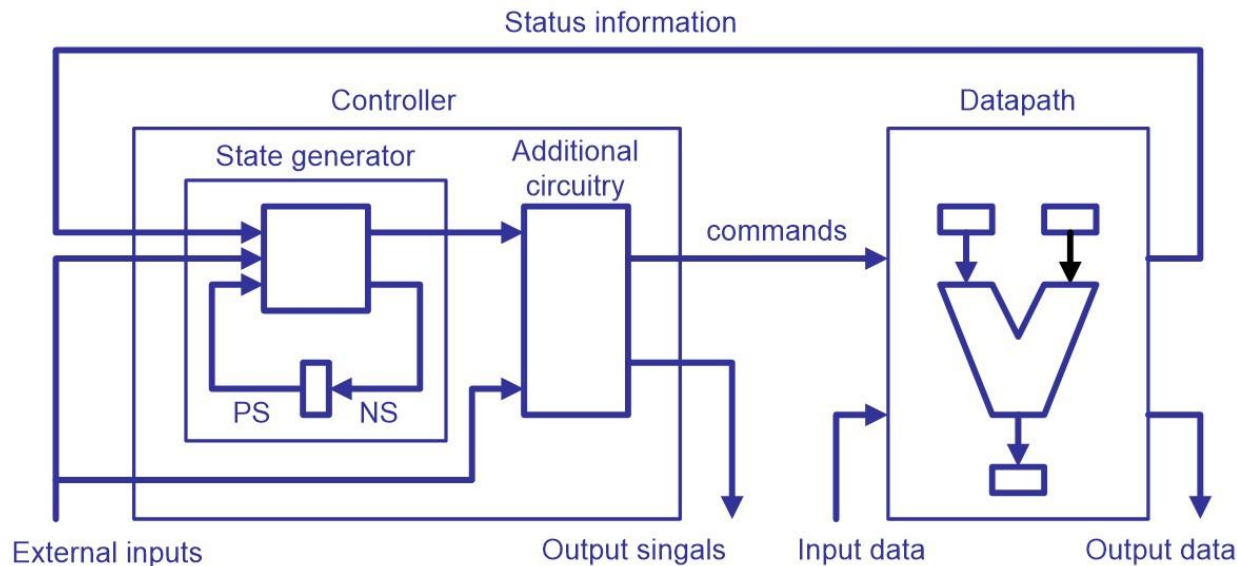
# FSMD Blocks

- Control Unit (FSM): States, transitions, outputs
- Datapath: Registers, ALU, multiplexers, etc
- Control Signals: Arrows from Control Unit to Datapath
- Status Signals: Arrows from Datapath to Control Unit



# Components of FSMD & Functions

- **Datapath:** Performs arithmetic, logic, and memory operations using an ALU, registers, multiplexers, and memory units
- **Control Path:** Generates control signals based on state transitions
- **Interaction:** The control unit determines the sequence of operations executed in the datapath

# Comparison

Feature	FSM (Finite State Machine)	FSMD (FSM with Datapath)
Definition	Controls system behavior using states and transitions	Includes both control logic and arithmetic operations
Datapath	No arithmetic or logical computations	Contains ALU, registers, and multiplexers
Operations	Simple state transitions	Performs complex arithmetic and logical operations
Control	State-based transitions	State-based transitions + datapath control
Applications	Sequential logic control, vending machines	Digital signal processing, embedded systems
Example	Traffic light controller	FIR filter, encryption processor

# Register Transfer (RT) Operation

- The movement of data between registers and the operations performed on that data
- Representation:
  - Use simple RT notation (e.g.,  $R1 \leftarrow R2 + R3$ )
- Example:
  - "Load data from memory to register R1"
  - "Add the contents of registers R2 and R3, store the result in R4"
  - "Shift the contents of register R5 left by one bit"



# FSMD Example: Counter

```
1  module fsmd_counter(  
2      input clk,  
3      input rst,  
4      output reg [3:0] count  
5  );  
6      reg [1:0] state;  
7      parameter S0 = 2'b00, S1 = 2'b01;  
8  
9      always @(posedge clk or posedge rst) begin  
10         if (rst) begin  
11             state <= S0;  
12             count <= 4'b0000;  
13         end else begin  
14             case (state)  
15                 S0: if (count < 4'b1111) begin count <= count + 1; state <= S1; end  
16                 S1: state <= S0;  
17             endcase  
18         end  
19     end  
20 endmodule
```

# FSMD Example: Counter\_Testbench

```
module fsmd_counter_tb;
    reg clk, rst;
    wire [3:0] count;


    fsmd_counter uut (.clk(clk), .rst(rst), .count(count));

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        rst = 1;
        #10 rst = 0;
        #100 $finish;
    end

    initial begin
        $monitor("Time=%0d, Count=%b", $time, count);
    end
endmodule
```

# FSMD Example: Adder\_Subtractor

 

IDLE:

- Waits for a valid operation (00 or 01)
- Transitions to CALCULATE

CALCULATE:

- Performs the add/sub and stores in **temp\_result**
- Moves to DONE

DONE:

- Transfers **temp\_result** to final output result.
- Goes back to IDLE.

# FSMD Code Breakdown: Adder\_Subtractor

## State Definitions

```
parameter IDLE = 2'b00;  
parameter CALCULATE = 2'b01;  
parameter DONE = 2'b10;
```

## Next State Logic

```
always @(*) begin  
    case (current_state)  
        IDLE:      → go to CALCULATE if operation is valid  
        CALCULATE: → go to DONE  
        DONE:      → go back to IDLE  
    endcase  
end
```

## Control Unit

State Register (Clocked always block)

```
always @(posedge clk)
```

Updates current\_state on every clock cycle

Resets to IDLE when reset = 1

# FSMD Code Breakdown: Adder\_Subtractor

## Datapath (Operations block)s

```
if (current_state == CALCULATE)
```

- ✓ Does the math ( $a + b$  or  $a - b$ )
- ✓ Stores in temp\_result (a 9-bit register)

```
✓ if (current_state == DONE)  
    result <= temp_result;
```

- ✓ On DONE state, updates the output result.

# FSMD Example: Adder\_Subtractor

```
1  module fsmd_adder_subtractor(  
2      input clk,  
3      input rst,  
4      input mode, // 0 for addition, 1 for subtraction  
5      input [3:0] A, B,  
6      output reg [3:0] result );  
7      reg [1:0] state;  
8      parameter IDLE = 2'b00, COMPUTE = 2'b01, DONE = 2'b10;  
9  
10     always @(posedge clk or posedge rst) begin  
11         if (rst) begin  
12             state <= IDLE;  
13             result <= 4'b0000;  
14         end else begin  
15             case (state)  
16                 IDLE: state <= COMPUTE;  
17                 COMPUTE: begin  
18                     if (mode == 0) result <= A + B;  
19                     else  
20                         result <= A - B; state <= DONE;  
21                 end  
22                 DONE: state <= IDLE;  
23             endcase  
24         end  
25     end  
26 endmodule
```

# FSMD Example: Adder\_Subtractor\_Testbench

```
module fsmd_adder_subtractor_tb;
    reg clk, rst, mode;
    reg [3:0] A, B;
    wire [3:0] result;

    fsmd_adder_subtractor uut (.clk(clk), .rst(rst), .mode(mode), .A(A), .B(B), .result(result));

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        rst = 1; A = 4'b0101; B = 4'b0011; mode = 0; // Addition
        #10 rst = 0;
        #20 mode = 1; // Subtraction
        #40 $finish;
    end

    initial begin
        $monitor("Time=%0d, Mode=%b, A=%b, B=%b, Result=%b", $time, mode, A, B, result);
    end
endmodule
```

# Summary

- FSMD provides a structured approach for digital design
- Used in high-performance computing and embedded systems
- FSM enables step-by-step control of operations
- Datapath performs actual computation
- FSM + Datapath = complete control + computation system



# Verilog HDL: ASMD

# Introduction

- ASMD is graphical representation of a Finite State Machine with Datapath (FSMD)
- Describe and visualize the sequential operations of a digital system
- Bridges the gap between algorithmic description and hardware implementation
- Simplifies FSMD design, verification, and documentation


# Why use ASMD Charts?

- Provides a clear visual representation of control flow and data operations
- Helps organize complex sequential algorithms
- Facilitates the design of both control and Datapath components
- Improves communication between designers

 
# ASM Symbols

Three types of symbols used in ASM charts are as follows:



- Rectangle is used to represent **outputs not dependent on input conditions**, such as the flip-flop outputs
- Diamond or hexagon is associated with **conditional execution of operations**; for  $n$  inputs,  $2^n$  branches are possible
- Rectangle with rounded corners is used to yield the **conditional outputs** (dependent on inputs)



(a)

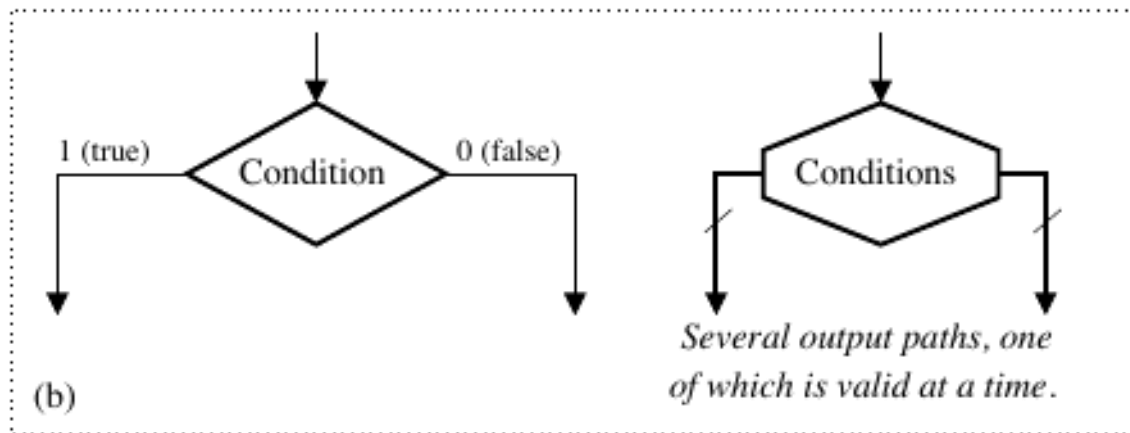


(b)

  


(c)


# Circuits & ASM Symbols

 


(a)

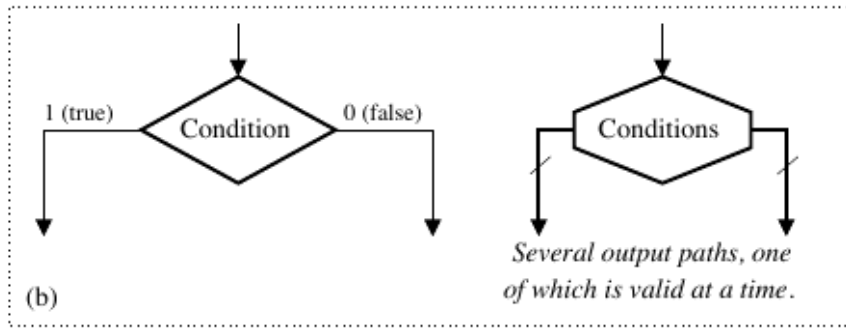



(b)

 

(c)


 


# ASM chart and logic circuits

 
 

  
# ASM chart and logic circuits

Caution needs to be exercised to avoid races; figure (a), below, admits races and should be avoided




# ASM chart and Moore m/c

  




# Example: Serial adder

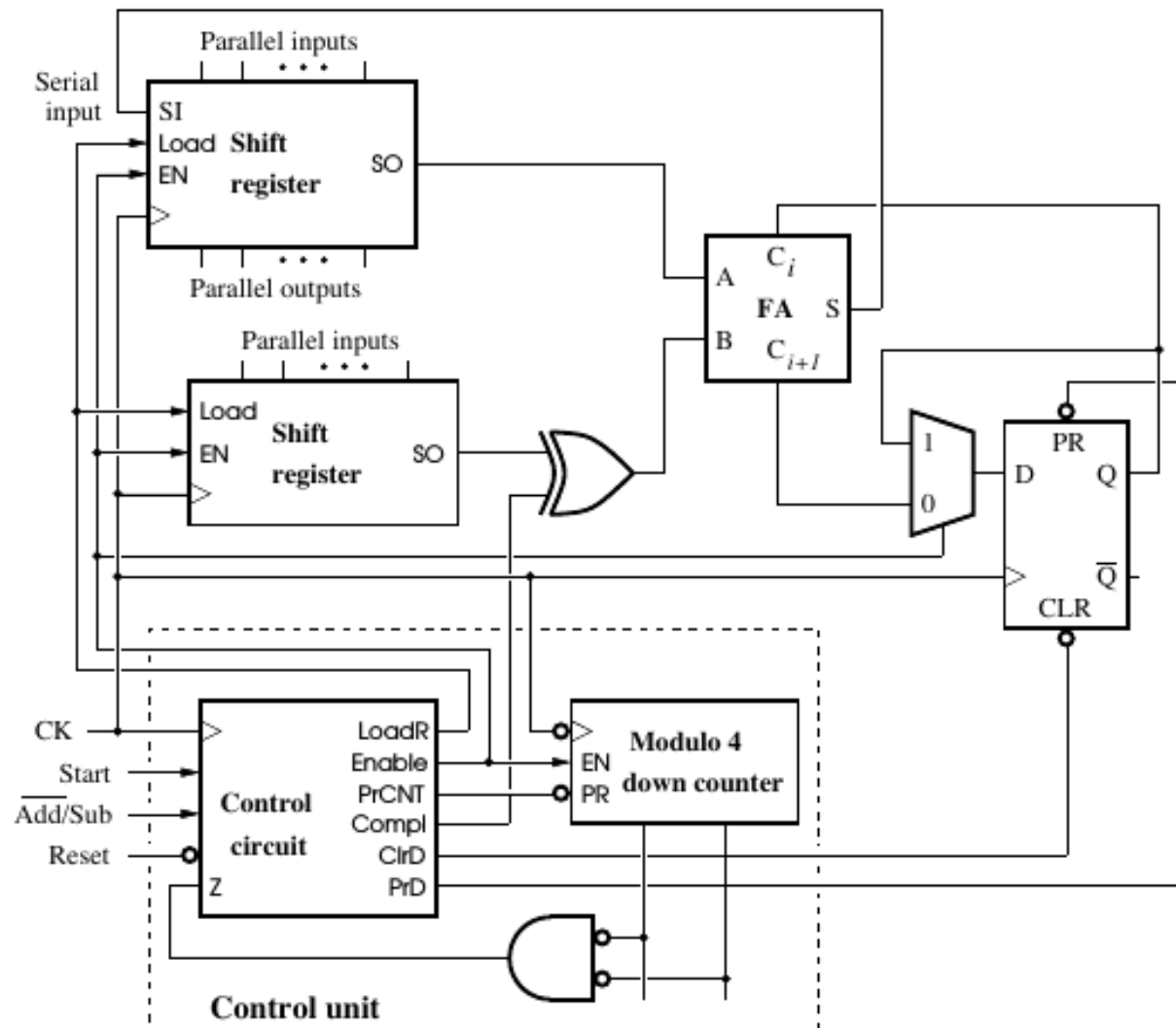

# Serial adder ASM chart

 



**Thank you !**

**Happy Learning**